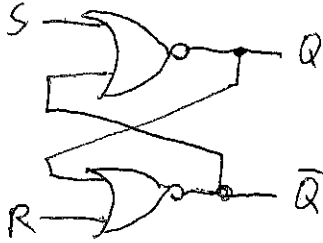



7.1



- If either input to a NOR is 1, the output must be 0, so if  $S=R=1$ ,  $Q=\bar{Q}=0$ .
- If  $S=1$ , then  $Q=0$ , and if  $R=0$ ,  $\bar{Q}=1$ .
- If  $R=1$ , then  $\bar{Q}=0$  and if  $S=0$ ,  $Q=1$ .

• If  $S=R=0$ , there are two stable outputs:  $Q=1$  and  $\bar{Q}=0$ , or  $Q=0$  and  $\bar{Q}=1$ .

7.2.

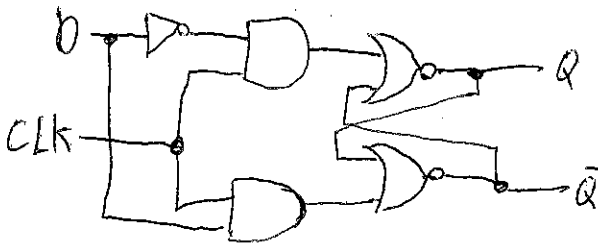

• This is different from the book's result because they reverse the positions of S and R (which is the standard NOR latch - but that's not obvious from the problem statement)



7.3.

Current state		next state	
g1	g0	d1	d0
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

$$a. d1 = g0 \oplus g1$$

$$d0 = \bar{g0}$$

b.

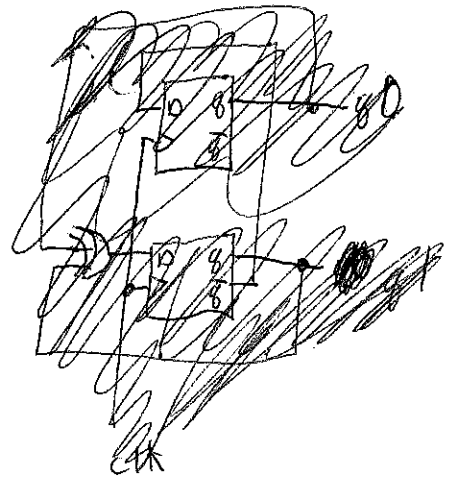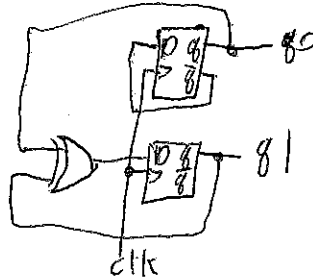


7.5

current state		next state	
g1	g0	d1	d0
0	0	1	0
0	1	1	1
1	0	0	1
1	1	0	0

$$a. d1 = \bar{g1}$$

$$d0 = g1 \oplus g0$$

b.

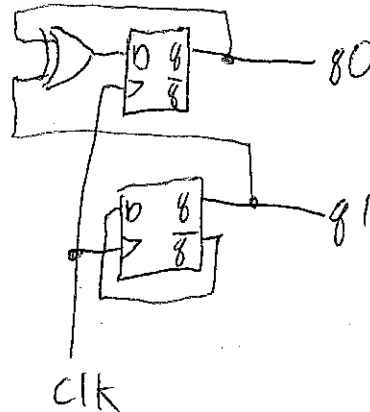


7.6

$q^3$	$q^2$	$q^1$	$q^0$
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1
0	0	0	0


$$D3 = \overline{q^0}, D2 = q^3, D1 = q^2, D0 = q^1$$

- 8.2.
- $s0$ : detected nothing correct
  - $s1$ : detected 1
  - $s2$ : detected 10
  - $s3$ : detected 101
  - $s4$ : detected 1010



Moore:

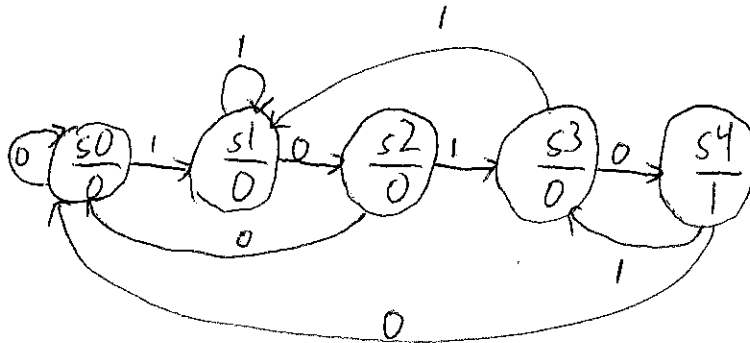



Mealy:

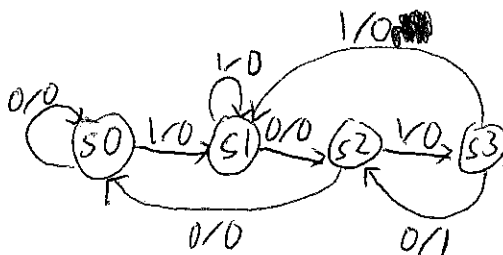

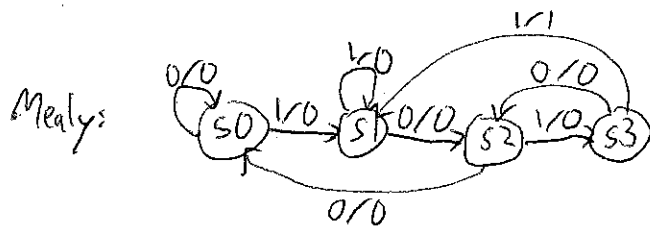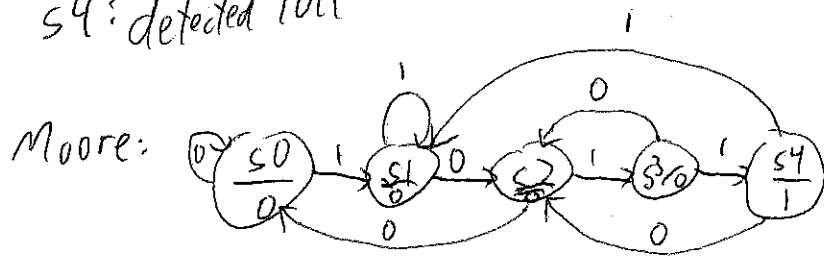8.3, s0: detected nothing correct  
 s1: detected 1  
 s2: detected 10  
 s3: detected 101  
 s4: detected 1011



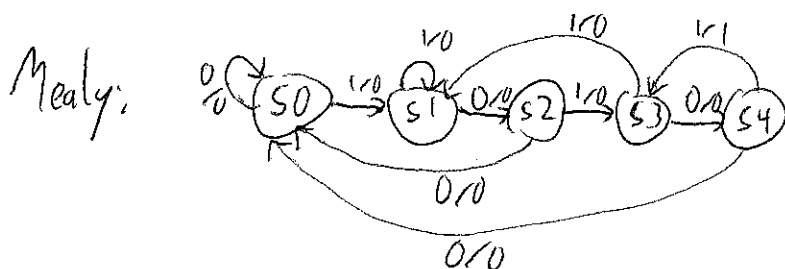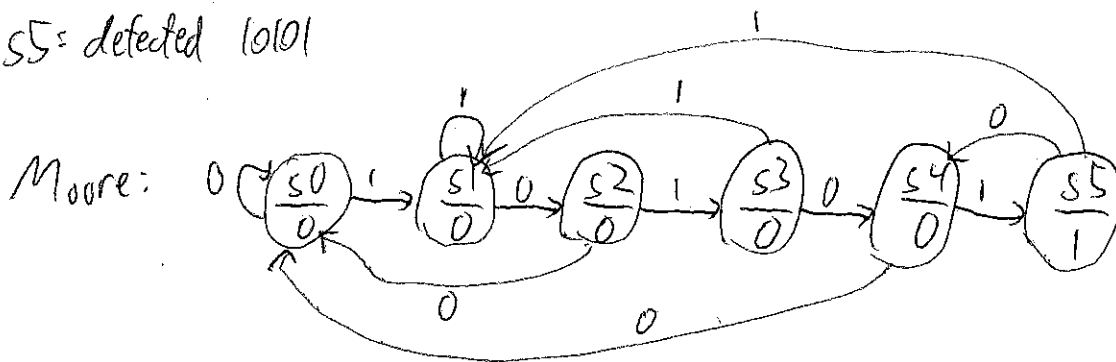8.4, s0: detected nothing correct  
 s1: detected 1  
 s2: detected 10  
 s3: detected 101  
 s4: detected 1010  
 s5: detected 10101



8.5

S0: detected nothing correct

S1: detected 1

S2: detected 11

S3: detected 110

S4: detected 1101

S5: detected 11011

